
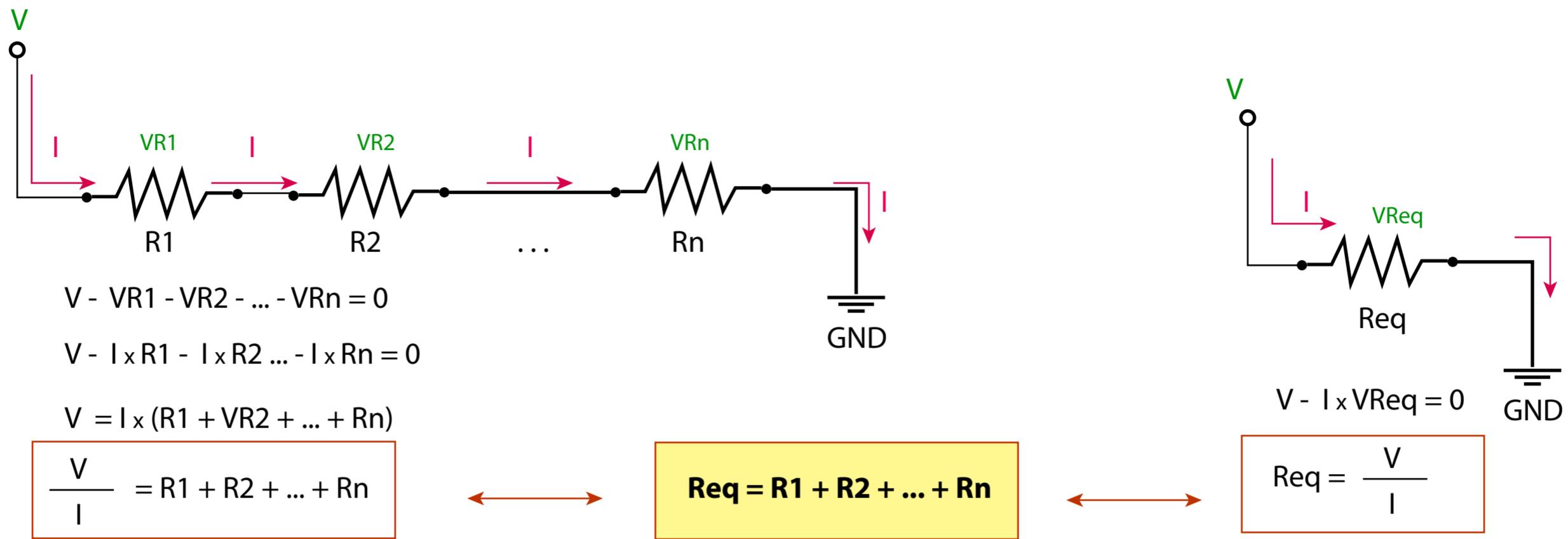


RESISTENCIAS EN SERIE

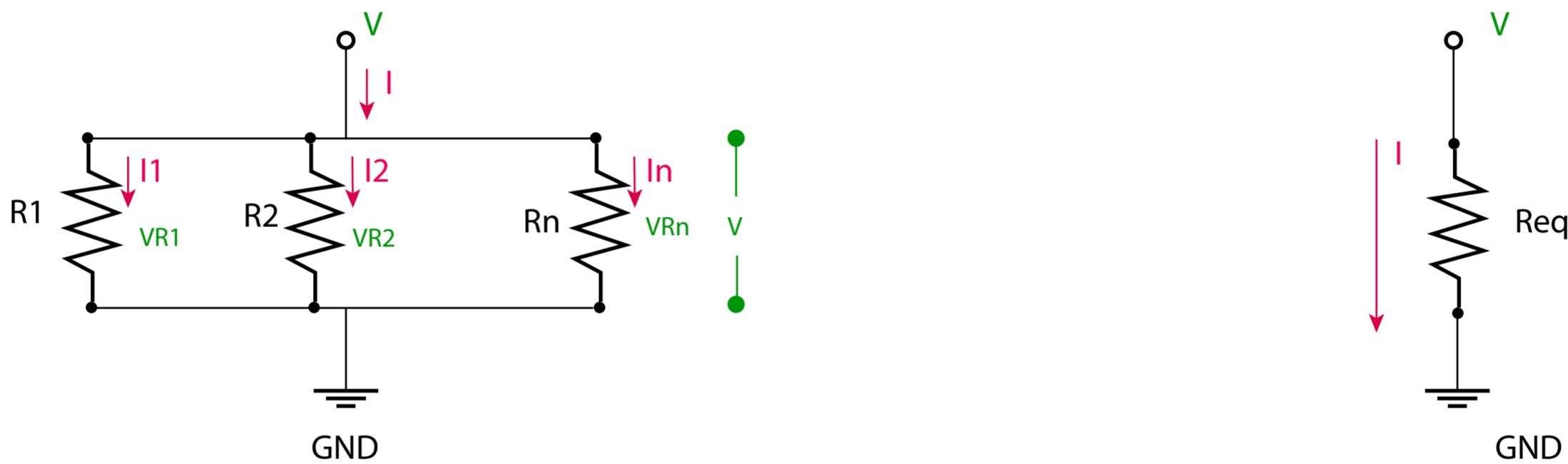

RESISTENCIAS EN PARALELO



$$\frac{1}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\frac{1}{Req} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$V = I \times Req$$

$$\frac{V}{I} = Req$$

$$\frac{I}{V} = \frac{1}{Req}$$